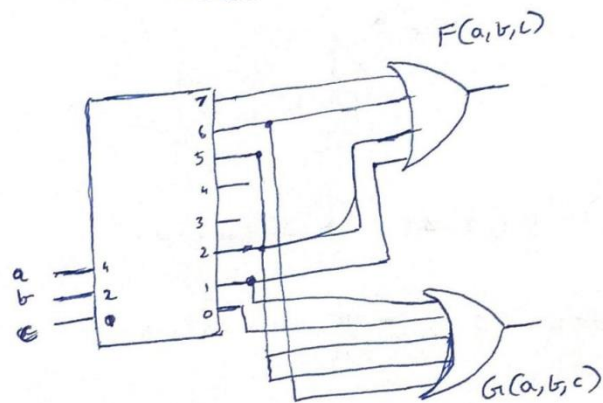


Ece home assignment CB.EN.U4CSE20465


1) $F(a,b,c) = \sum m(1,2,6,7)$ $G(a,b,c) = \sum m(0,1,2,5,6)$
functions F and G with single decoder

→ minterms of $F : 1, 2, 6, 7$ $G : 0, 1, 2, 5, 6$

We need 3×8 Decoder




with nand gate

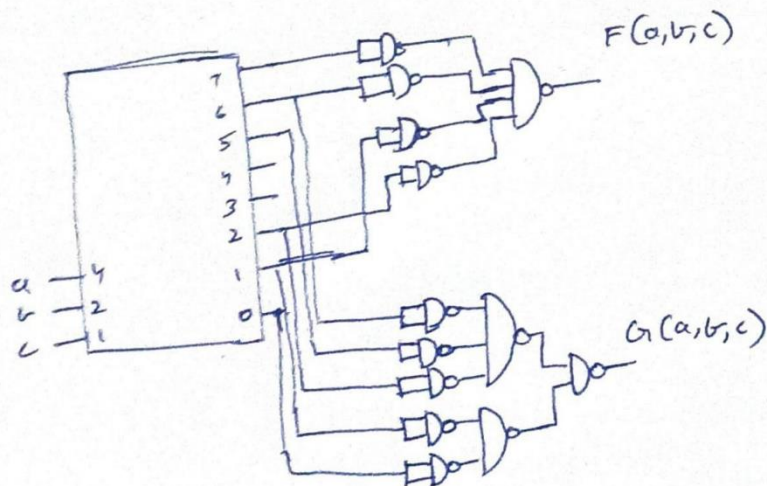


A-1 b-0 c-1 : 5


=> $f(a, b, c)$ should give 0

And $g(a, b, c)$ should give 1

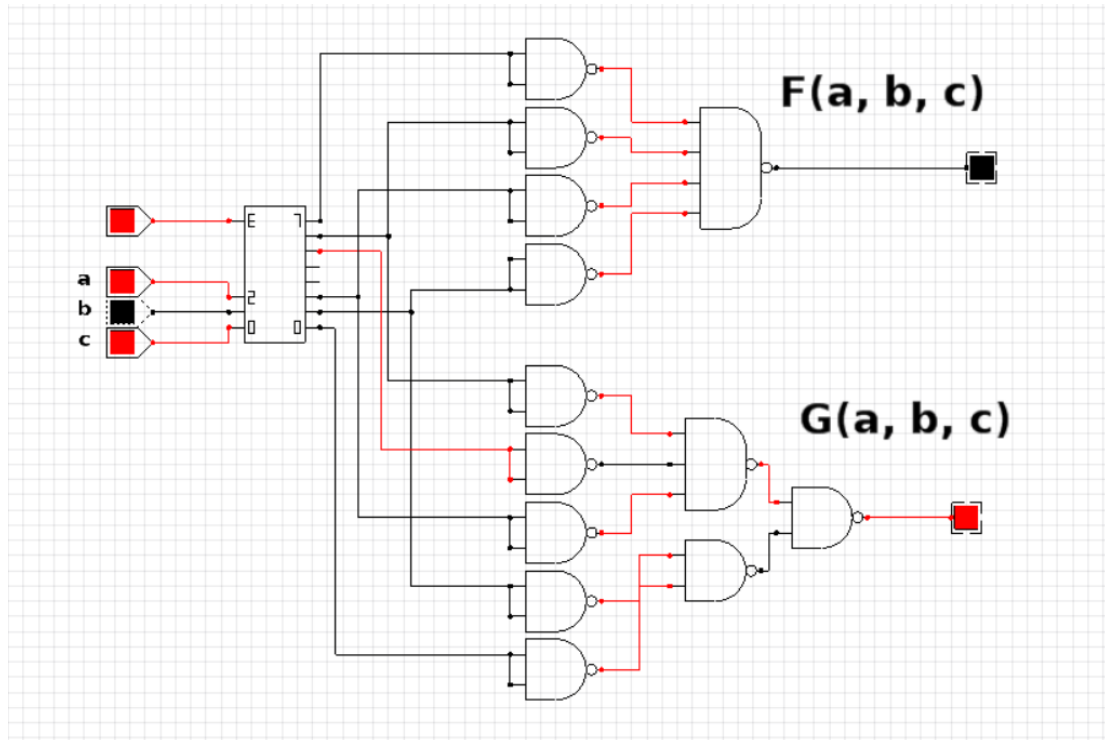


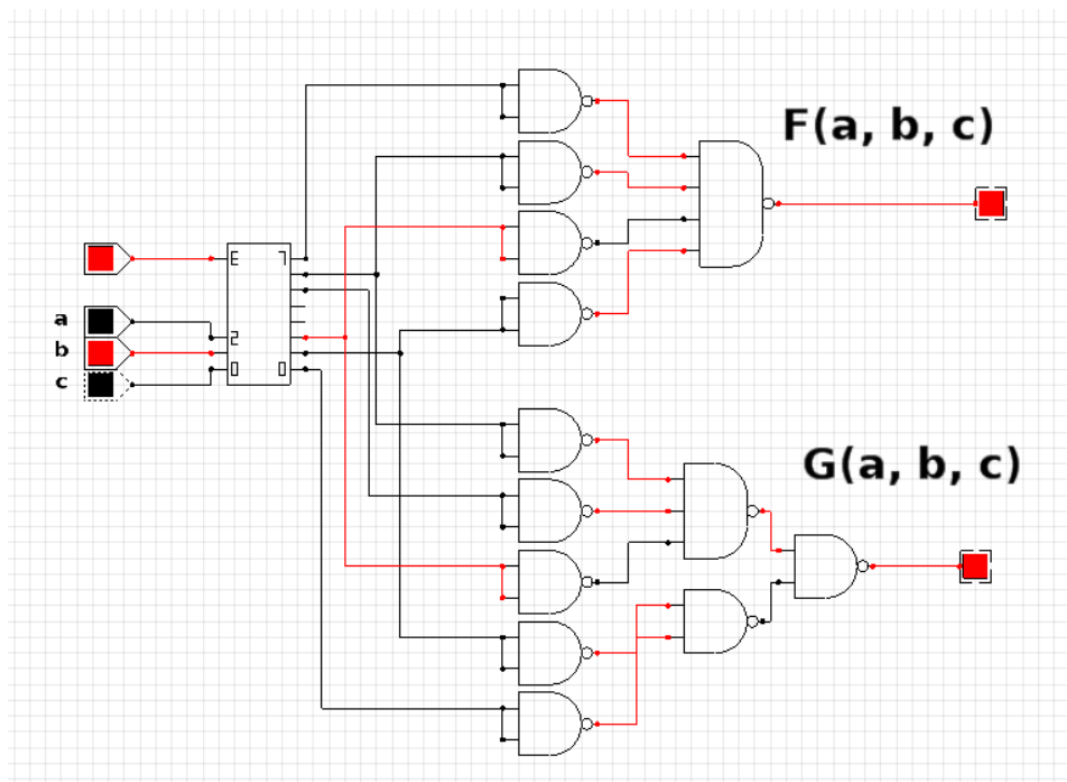A-0 b-1 c-0 : 2
 => f(a, b, c) should give 1
 And g(a, b, c) should give 1



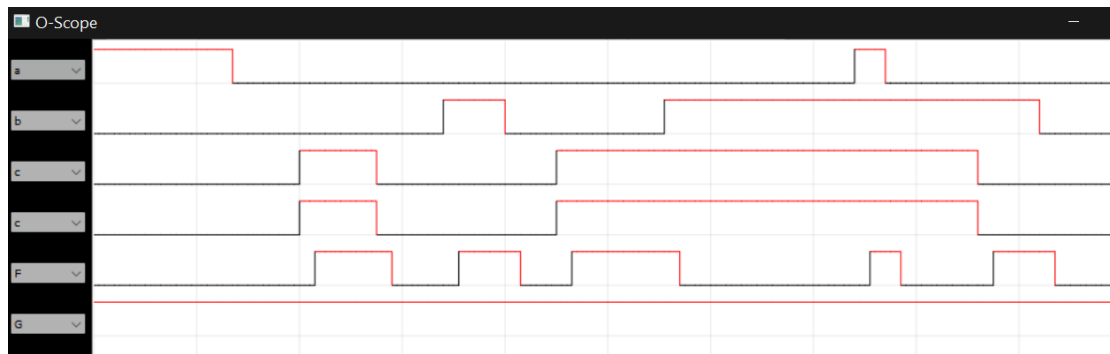

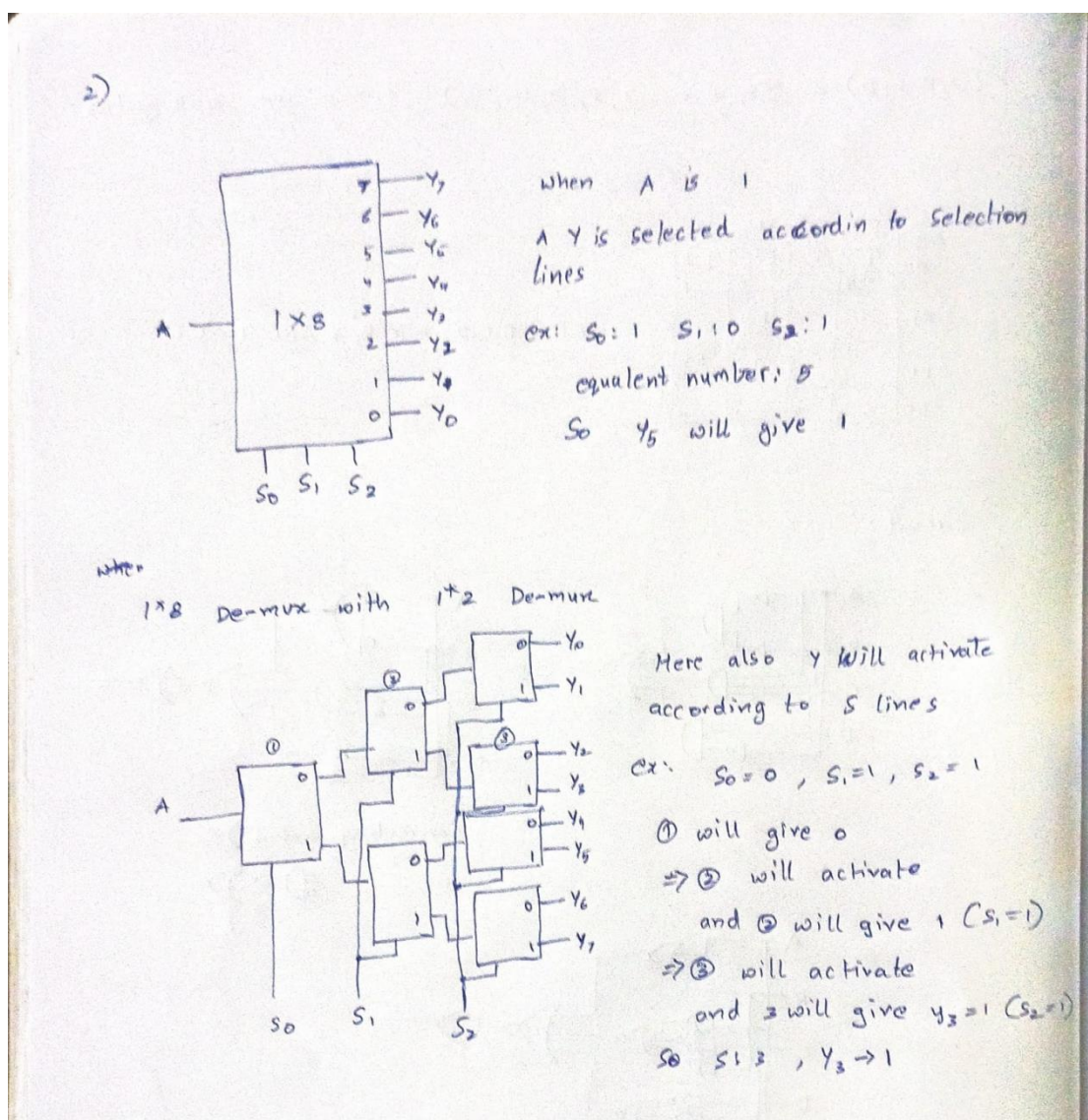
2. 1*8 de-mux and 1*8 de-mux from 1*2 de-mux



3.

A sequential circuit with two D flip-flops A and B, one input x, and one output z is specified by the following next state and output equations: $A(t+1) = A'B$, $B(t+1) = B'x$, $z = A+B'$. (i) Draw the logic diagram of the circuit. (ii) Derive the state table (iii) Draw the state diagram of the circuit and simulate its behavior using a simulation tool.

(i)

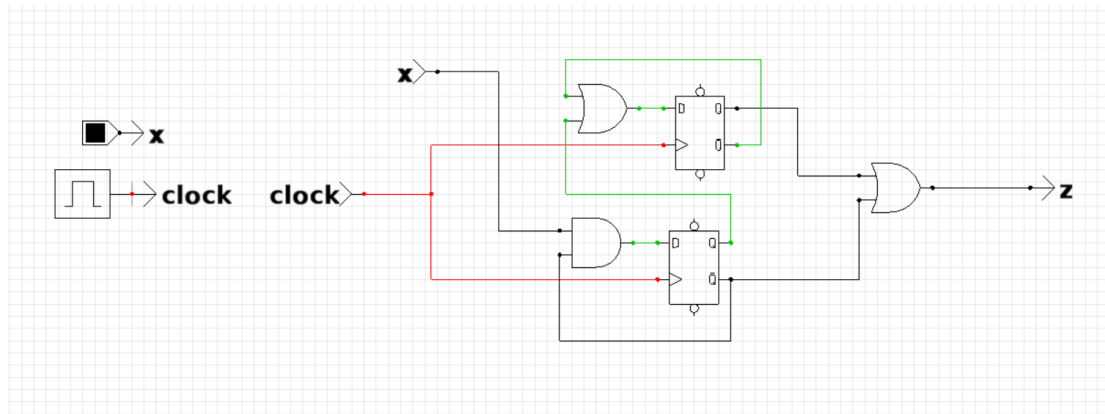



(ii)

State table

Present State	Next state		output
	$x=0$	$x=1$	
BA	BA	BA	Z
00	01	11	1
01	00	10	0
10	01	01	1
11	01	01	1


BA	BA		Z
	$x=0$	$x=1$	
A	B	D	1
B	A	C	0
C	B	B	1
D	B	B	1

(iii)

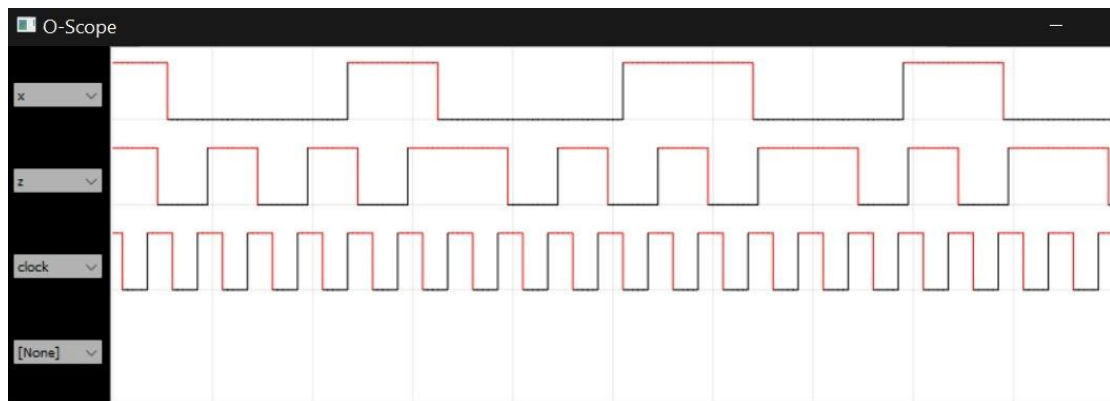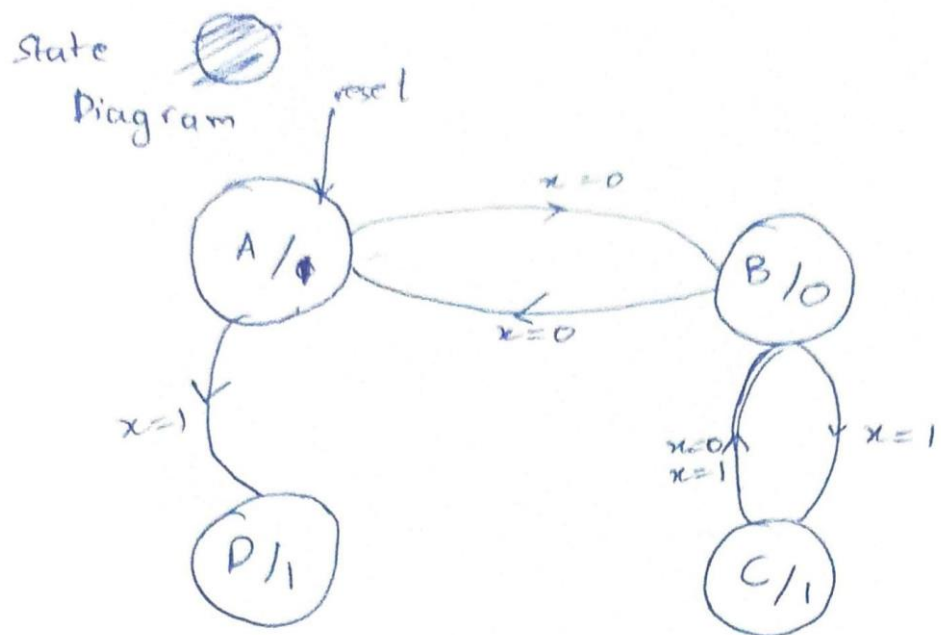


Design a circuit using a single ripple adder for computing the value of y given $y = 9x$, where x is an 8-bit number. Simulate for four different values of x .


4.

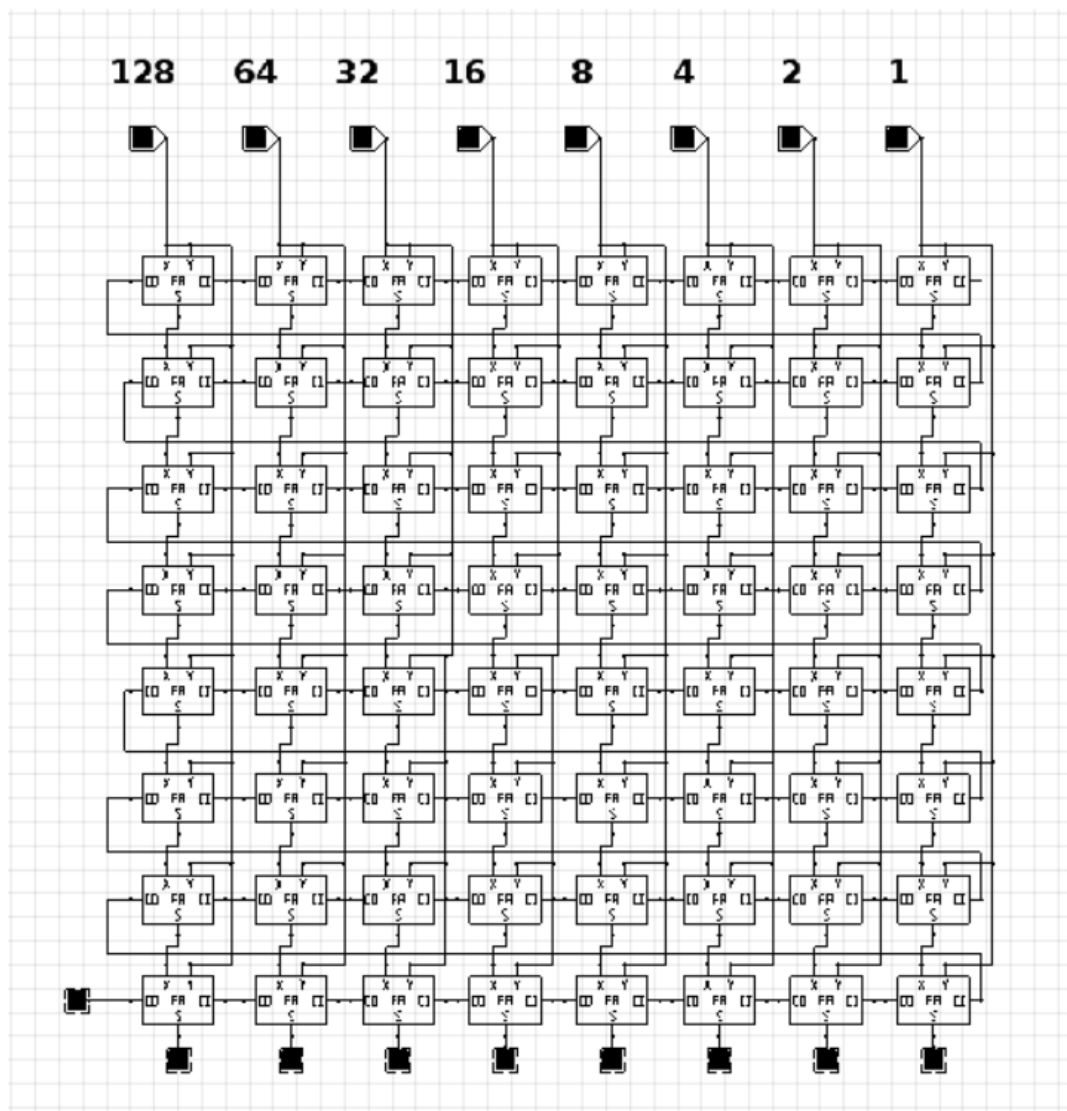


When input is 16, output is 144

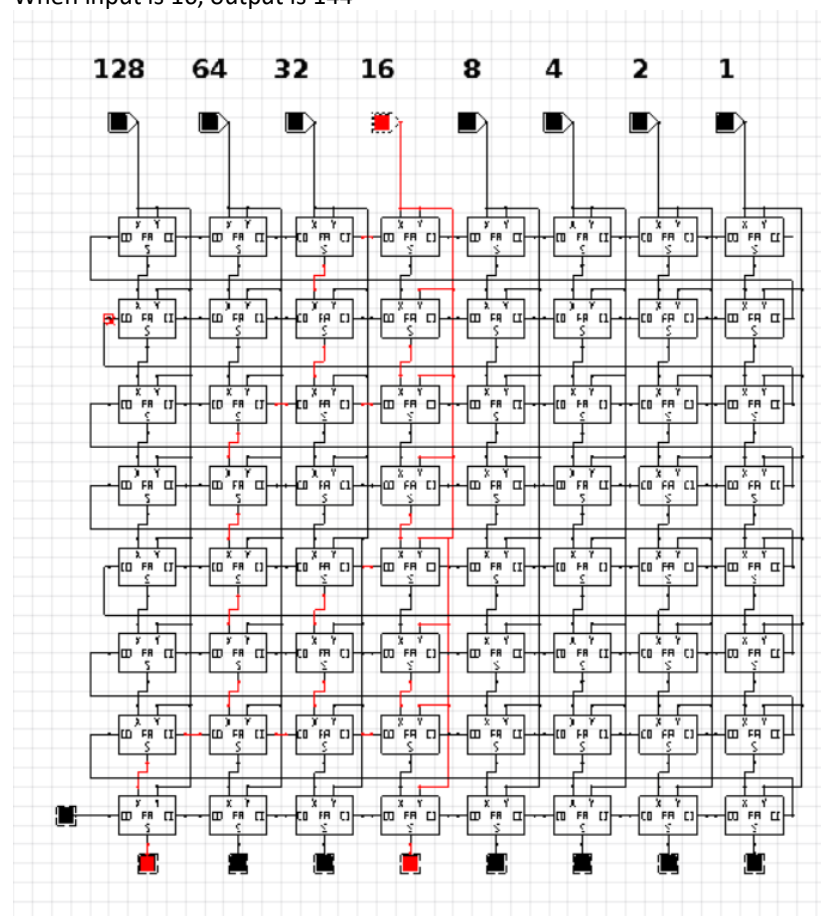


When input is 3, output is 27

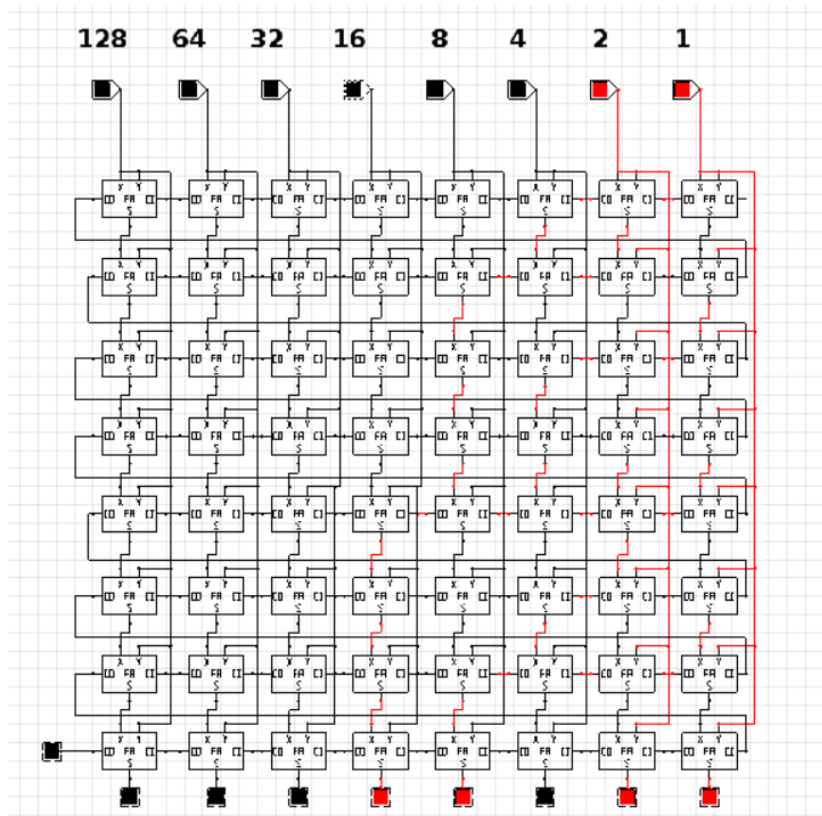

When input is 4, output is 36

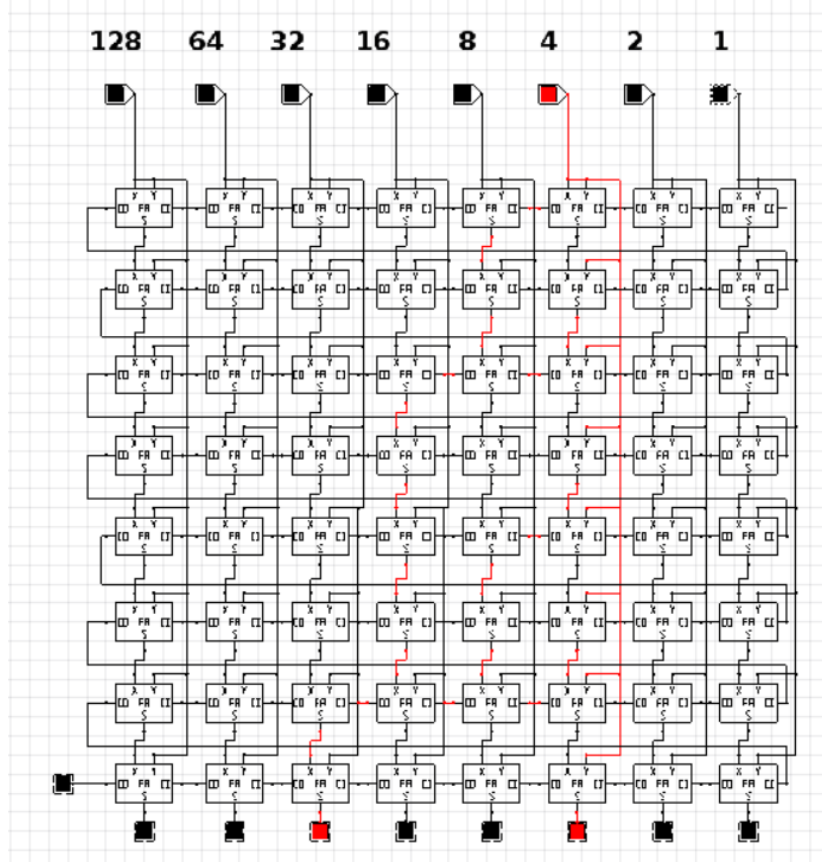

When input is 10, output is 90:

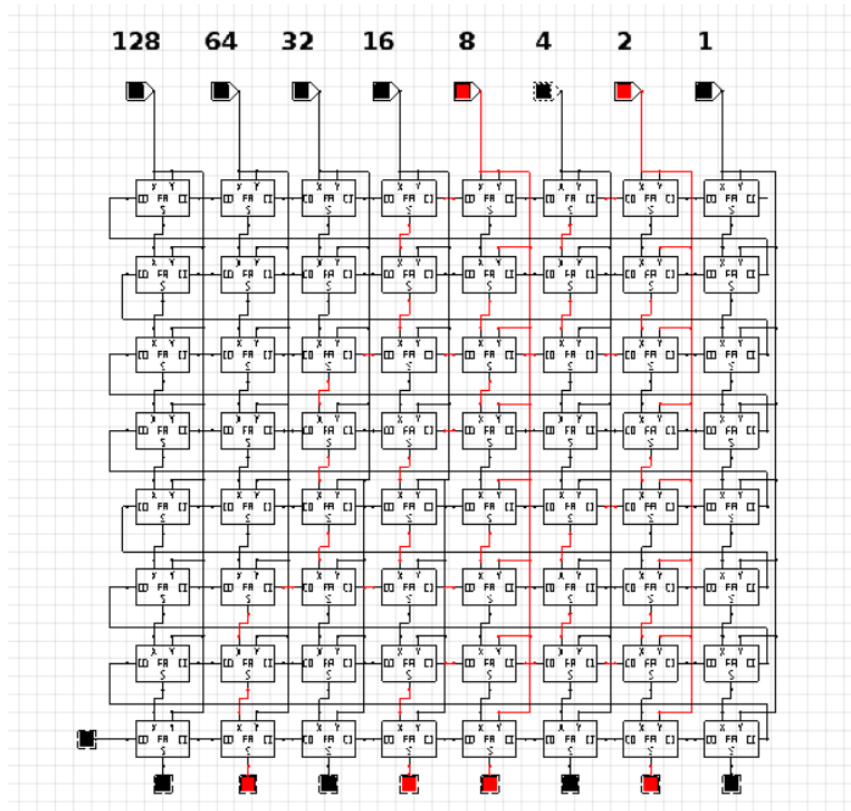


5.

5) $F(A, B, C, D) = \sum m(0, 1, 2, 3, 7, 14, 15)$, K map and NOR gates


	CD			
	00	01	11	10
AB	00	1	1	1
	01		1	
	11			1
	10			

$$\Rightarrow F(A, B, C, D) = A'B' + ABC + A'CD$$

circuit:

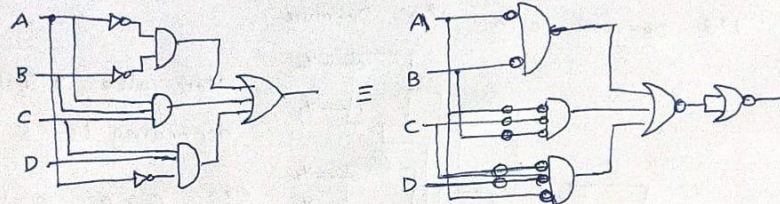


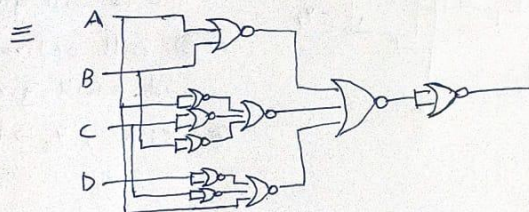Converting $\square \rightarrow \square$
 $\square \rightarrow \square$




When

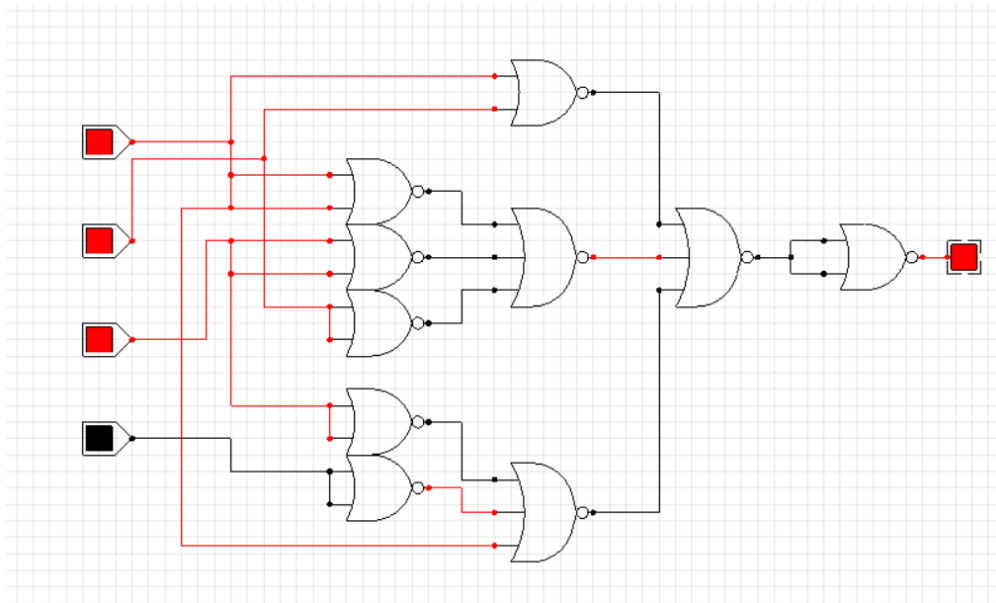A-1, B-1, C-1, D-0 \Rightarrow 14 output should be 1



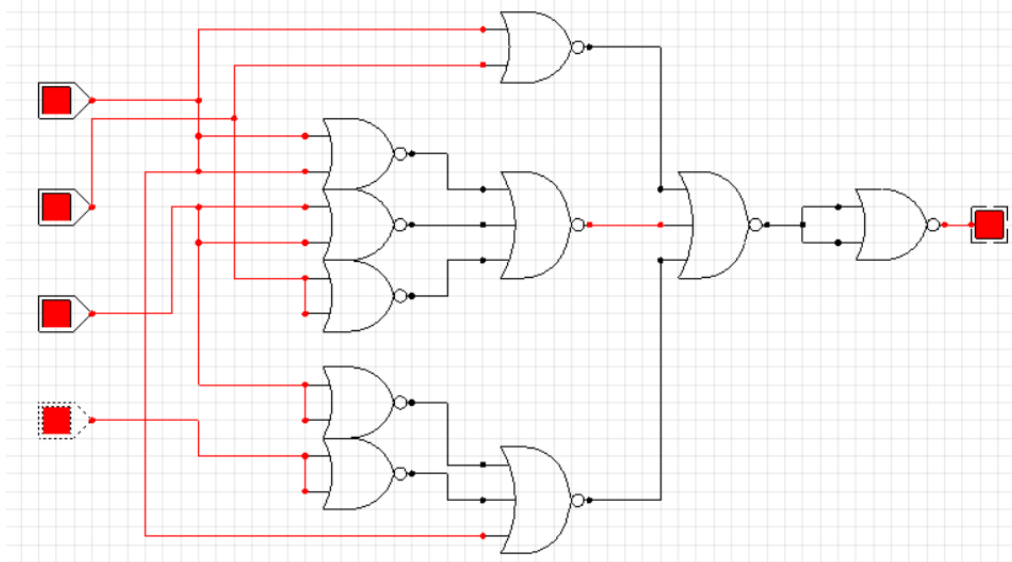A-1, B-1, C-1, D-1 => 15 output should be 1



A-1, B-0, C-0, D-0 => 8 output should be 0

